

# **Modeling and Simulation of Power Electronics Converters**

**Chun Wei**

Simulation content:

- 1. Modeling and simulation of buck circuit in CCM mode**
2. Modeling and simulation of three-phase voltage source PWM inverter

$$L \frac{d\hat{i}(t)}{dt} = -DR_g \hat{i}(t) - \hat{v}(t) + D\hat{v}_g(t) + (V_g - R_g I) \hat{d}(t)$$

$$C \frac{d\hat{v}(t)}{dt} = \hat{i}(t) - \frac{1}{R} \hat{v}(t)$$

$$i_g(t) = D\hat{i}(t) + I\hat{d}(t)$$


# 1. Modeling and simulation of buck-boost circuit in CCM mode

The small signal AC model of buck-boost converter is as follows

$$L \frac{d \hat{i}(t)}{dt} = D \hat{v}(t) + D' \hat{v}(t) + (V_g - V) \hat{d}(t)$$



$$C \frac{d \hat{v}(t)}{dt} = -D' \hat{i}(t) - \frac{\hat{v}(t)}{R} + I \hat{d}(t)$$
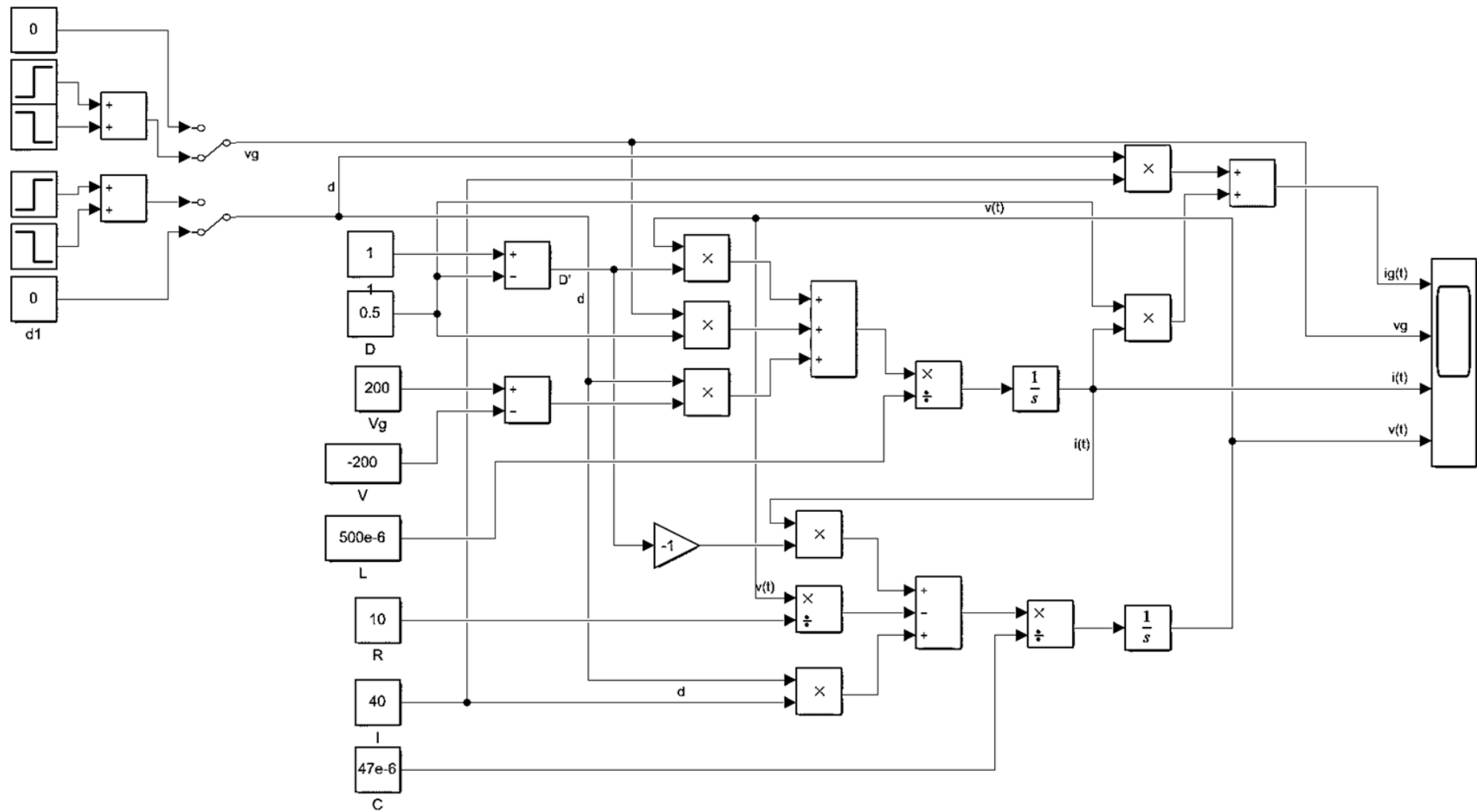
$$\hat{i}_g(t) = D \hat{i}(t) + I \hat{d}(t)$$



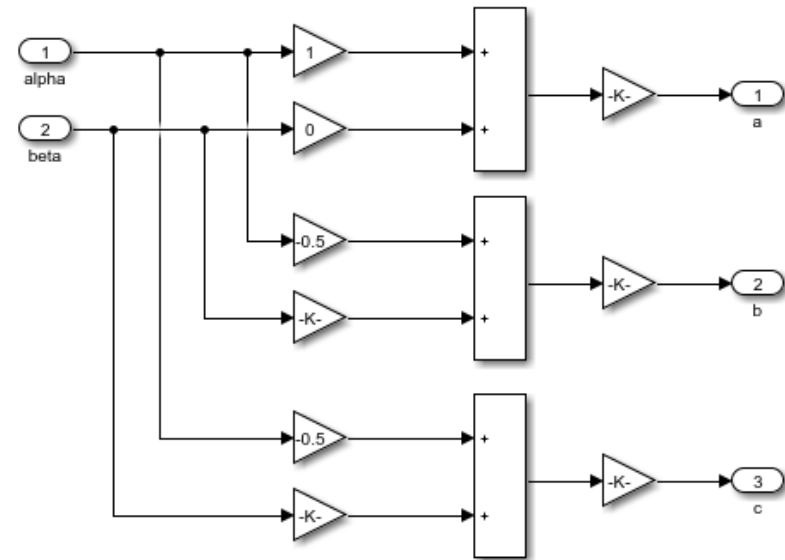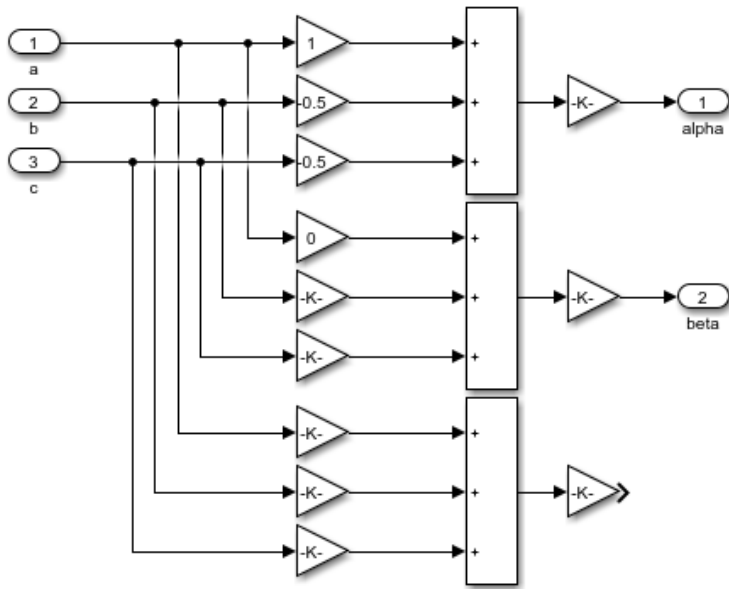
### 3. Modeling and simulation of three-phase voltage source PWM inverter


$$\begin{cases} \frac{d}{dt} \begin{bmatrix} \langle i_d \rangle_{T_s} \\ \langle i_q \rangle_{T_s} \end{bmatrix} = -\frac{1}{3L} \begin{bmatrix} \langle v_d \rangle_{T_s} \\ \langle v_q \rangle_{T_s} \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \langle i_d \rangle_{T_s} \\ \langle i_q \rangle_{T_s} \end{bmatrix} + \frac{1}{3L} \begin{bmatrix} d_d \\ d_q \end{bmatrix} \cdot \langle v_{dc} \rangle_{T_s} \\ \frac{d}{dt} \begin{bmatrix} \langle v_d \rangle_{T_s} \\ \langle v_q \rangle_{T_s} \end{bmatrix} = \frac{1}{C} \begin{bmatrix} \langle i_d \rangle_{T_s} \\ \langle i_q \rangle_{T_s} \end{bmatrix} - \begin{bmatrix} 0 & -\omega \\ \omega & 0 \end{bmatrix} \cdot \begin{bmatrix} \langle v_d \rangle_{T_s} \\ \langle v_q \rangle_{T_s} \end{bmatrix} - \frac{1}{RC} \begin{bmatrix} \langle v_d \rangle_{T_s} \\ \langle v_q \rangle_{T_s} \end{bmatrix} \\ \langle i_{dc} \rangle_{T_s} = \begin{bmatrix} d_d & d_q \end{bmatrix} \cdot \begin{bmatrix} \langle i_d \rangle_{T_s} \\ \langle i_q \rangle_{T_s} \end{bmatrix} \end{cases}$$



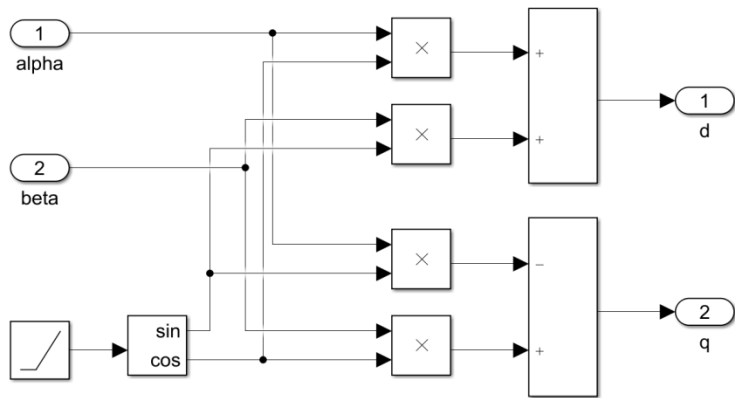
(a) Clark transform simulation diagram      (b) Clark inverse transformation simulation diagram



(a) Park transform simulation diagram

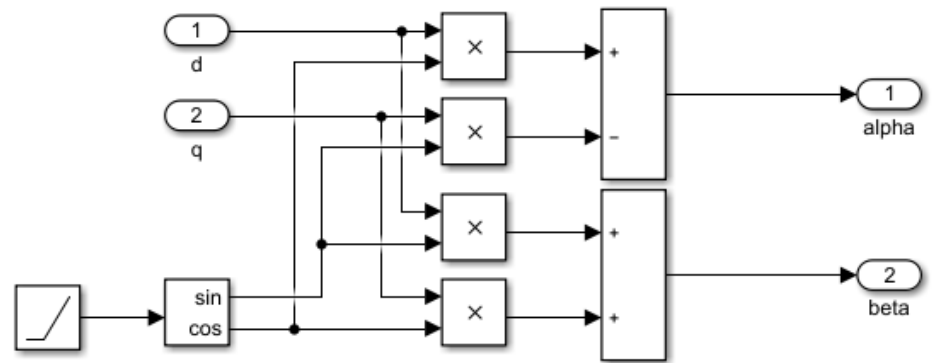

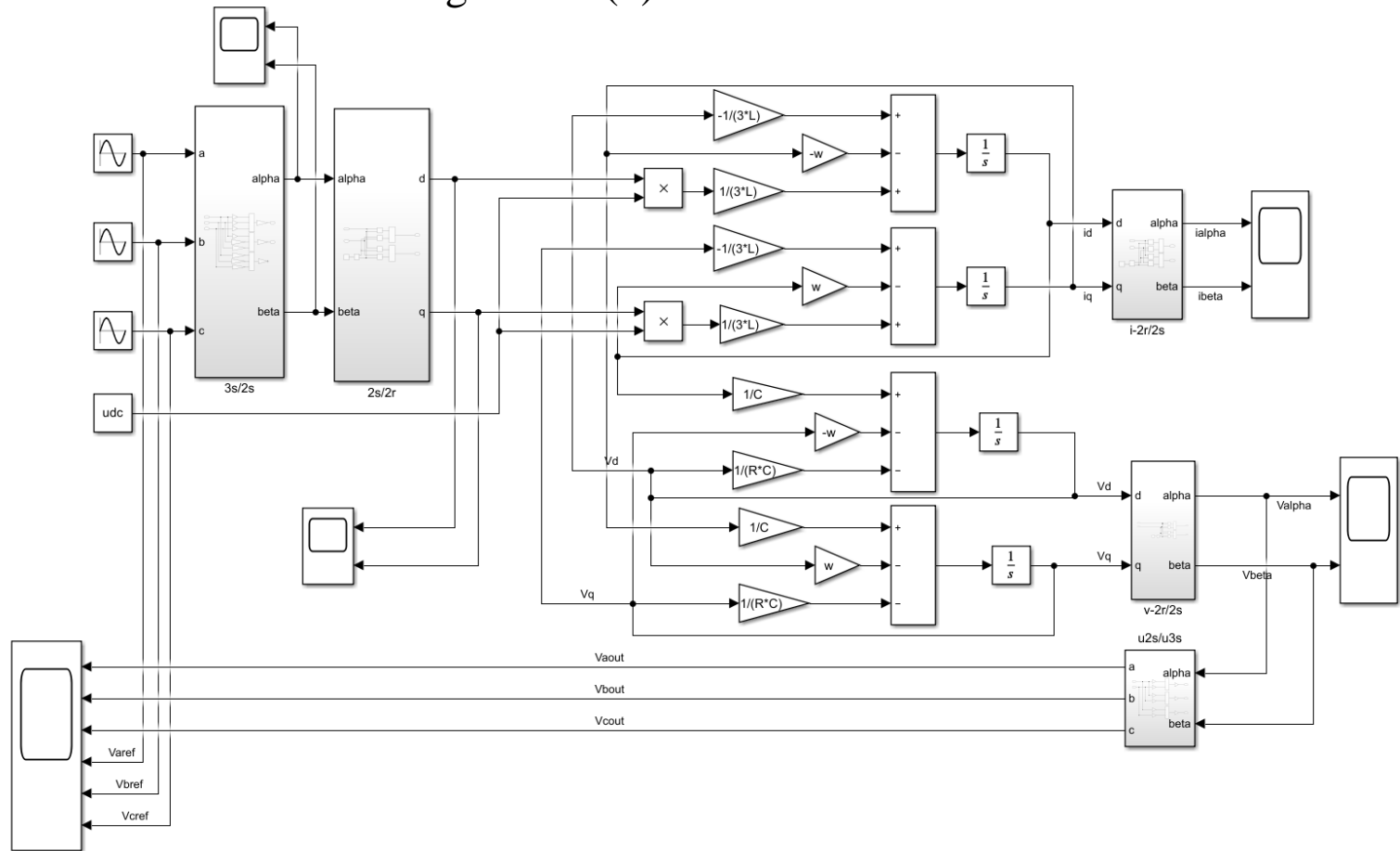(b) Park inverse transformation simulation diagram



# 英文实验报告要求

1月17日上交

全英文电子稿报告+仿真模型

jiangyongkai@zjut.edu.cn

要素:

□ 标题:

□ 作者: 姓名、班级、学号

□ 正文: 实验内容, 实验方法, 仿真结果.....

格式要求:

□ 标题: 醒目、各级标题大小不同

□ 正文: 中文宋体/英文Times New Roman, 小4号, 1.2倍行间距, 段前空2格; 图、表标题不可缺。

# 英文小论文要求

和实验报告一起，1月17日上交  
jiangyongkai@zjut.edu.cn

主题： 结合自己的科研内容+电力电子相关技术

格式要求：

IEEE 期刊论文格式：标题、作者、摘要、引言、研究内容、研究方法、分析、结论、参考文献。

清晰美观